



Subject: - Circuits and Networks ( 2130901)

Date:- 15/09/2014

Total Marks:-30

Time: - 75 Minutes

**Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

**Question: 1.**

[6 x 1]

Explain Non-Linear element, Time Invariant element and Lumped element with examples. And find out the equivalent inductance across points a and b in the **Figure 1**.

**Question: 2.**

[6 x 2]

- (a) Find out the THEVENIN'S equivalent circuit across points A and B in the **Figure 2**.
- (b) Find individual MESH CURRENTS in **Figure 3**.

**OR**

- (a) Find the NORTON equivalent across points A and B in given **Figure 4**.
- (b) Find the individual NODE VOLTAGES in **Figure 5**.

**Question: 3.**

[6 x 2]

- (a) Find the voltage across the 1 Ohm resistor in **Figure 6** using SUPER POSITION theorem.
- (b) Find the Z parameter for the network given in **Figure 7**.

**OR**

- (a) For the magnetically coupled circuit shown in **Figure 8**, Find DOT Convention and write MESH equations.
- (b) Find the Z parameter for the network given in **Figure 9**.

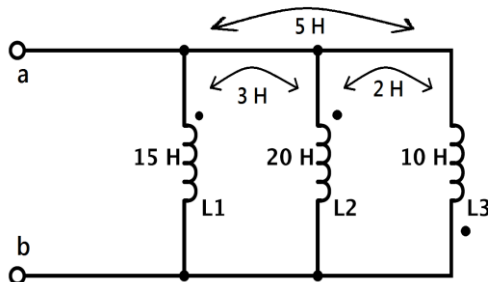
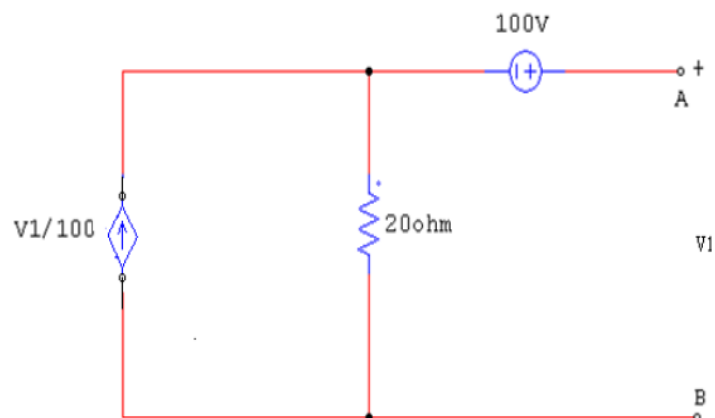
**Figure 1****Figure 2**

Figure 3

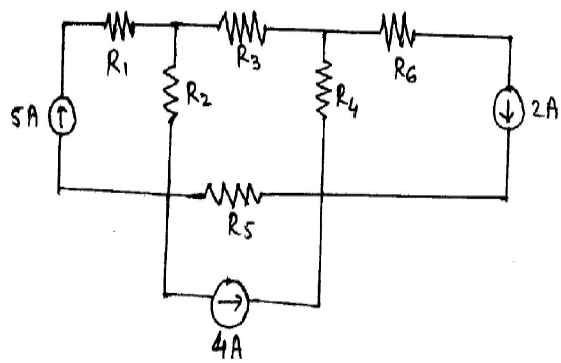


Figure 4

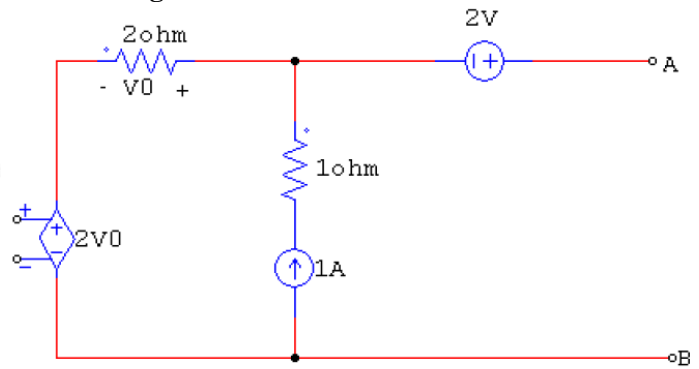


Figure 5

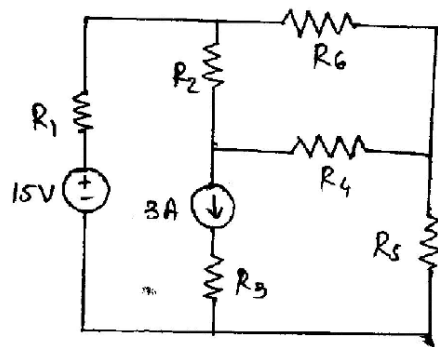


Figure 6

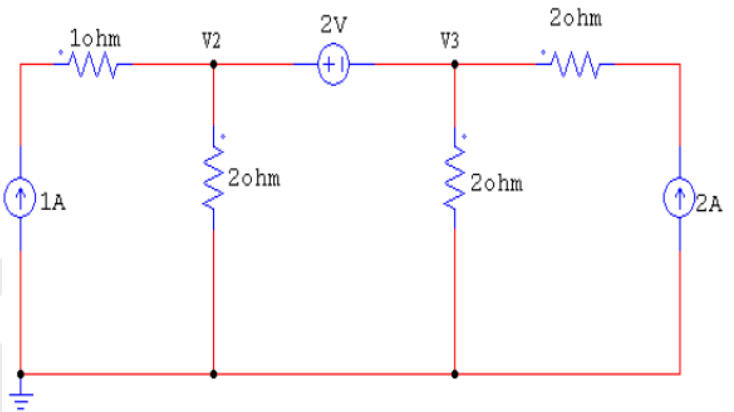


Figure 7

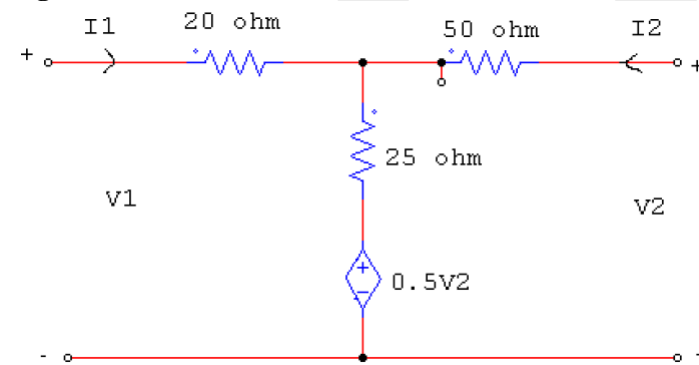


Figure 8


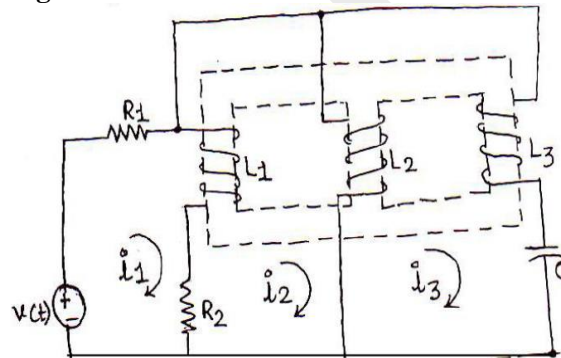


Figure 9

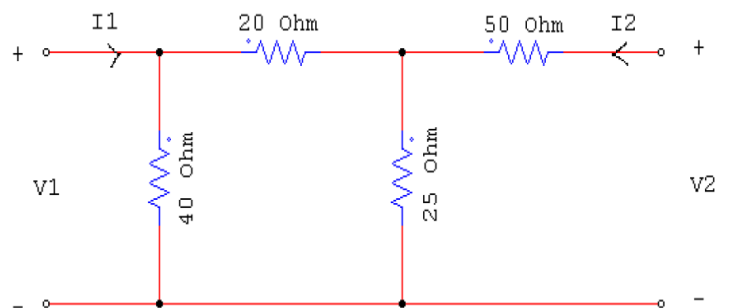

ALL THE BEST !!!

## Course Outcome Wise Questions

Subject Code	<b>2130901</b>	Subject	<b>CIRCUITS &amp; NETWORKS</b>
--------------	----------------	---------	--------------------------------

CO No.	Course Outcome
<b>CO1</b>	Get knowledge of various network theorems like superposition, Thevenin's, Norton and more for circuit analysis.(Knowledge)
<b>CO2</b>	Understand mathematical transforms to describe the behavior of networks which are represented using differential equations.(Understand)
<b>CO3</b>	Application of knowledge for solving the electrical circuit problems using different methods. (Application)
<b>CO4</b>	Discuss methods of reducing the circuit. Develop an ability to choose an appropriate analytical method.(Analytical)
<b>CO5</b>	Develop the ability to design electrical circuits based on the given inputs and outputs.
<b>CO6</b>	Evaluate lecture material with circuit simulation software and laboratory bench experiments. (Evaluate)

Blooms Taxonomy	Question List
<b>Remember / Knowledge</b>	
<b>Understand</b>	
<b>Apply</b>	
<b>Analyze</b>	
<b>Evaluate</b>	
<b>Higher order Thinking / Creative</b>	